

Current Amps (A) → $I = \frac{\Delta Q}{\Delta t}$ ← Charge (c)
 ← Time (s)

Current = rate of flow of charge
 -electrons in a wire
 -electrons in beam
 -ions (beam/solution)

NB: Δ = small change in

$N = \frac{I}{q} = \frac{\text{charge/sec}}{q}$ → No. of ions/ sec

$E = ItV$

$E = I^2RT$

EMF: Electromotive force (E)

Potential Divider Circuits

If $R_1 = R_2$ then V_1 reads 2.5V
 V_2 reads 2.5V

As R_2 increases then V_2 increases & V_1 decreases
 $V_1 + V_2 \equiv 5V$

$\frac{V_2}{V_{in}} = \frac{R_2}{R_1 + R_2}$

$E = V^2 \times t$

Power (P) - Energy transferred per unit of time.

Any System → $P = \frac{\Delta E}{\Delta t}$

For electricity → $P = IV$

→ $P = \frac{V^2}{R}$

J/s - watt

Chapter 2 Sensing


Potential Difference - difference in energy per coulomb between two places in a circuit

$V = \frac{\Delta E}{\Delta Q}$

Energy transferred (J)
 Energy flowing (c)

No. of charge carriers → Drift → $I = nAvq$

P.d. J/c or Volts (V)

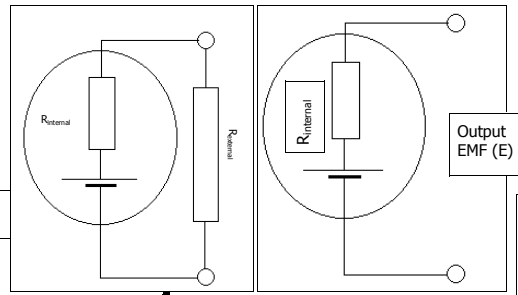

Source : Some resistance
 $I = \frac{E}{R_{\text{external}} + R_{\text{internal}}}$
 Output
 $V = I \times R_{\text{external}}$
 $= E - I \times R_{\text{internal}}$

Ohm's Law -resistance and conductance

- The conductance or resistance can be calculated at any given p.d.
- If the conductance or resistance are constant, independent of the current or p.d., the conductor is said to obey Ohm's law, or to be 'ohmic'.
- Ohm's law thus says that the conductance, and resistance, of a given component is constant. The same value can be used in calculations whatever the current or p.d.
- Most metals are ohmic at constant temp.; ionised gases are not.

See also Chapter 4

Source: High resistance
 $R_{\text{internal}} \approx \infty$
 $I \approx 0$
 Output
 $V = I \times R_{\text{external}} \approx 0$

Source: Low resistance
 $R_{\text{internal}} \approx 0$
 $I = \frac{E}{R_{\text{external}} + R_{\text{internal}}}$
 Output
 $V = I \times R_{\text{external}} \approx E$

$V = IR$

$R = \frac{V}{I}$

$G = G_1 + G_2 + G_3 \dots$
 $R = \frac{1}{G}$

$R = R_1 + R_2 + R_3 \dots$
 $G = \frac{1}{R}$